

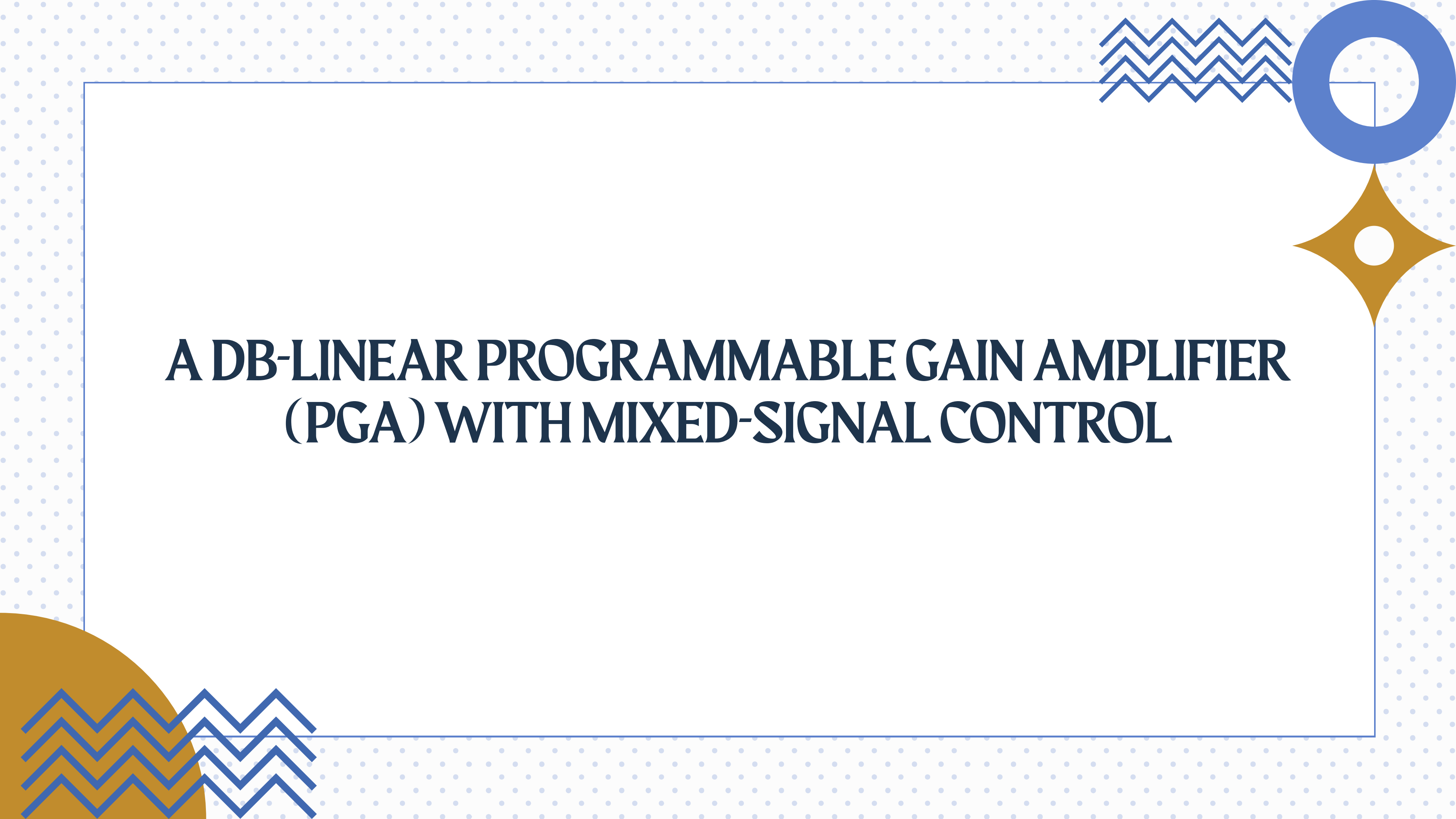


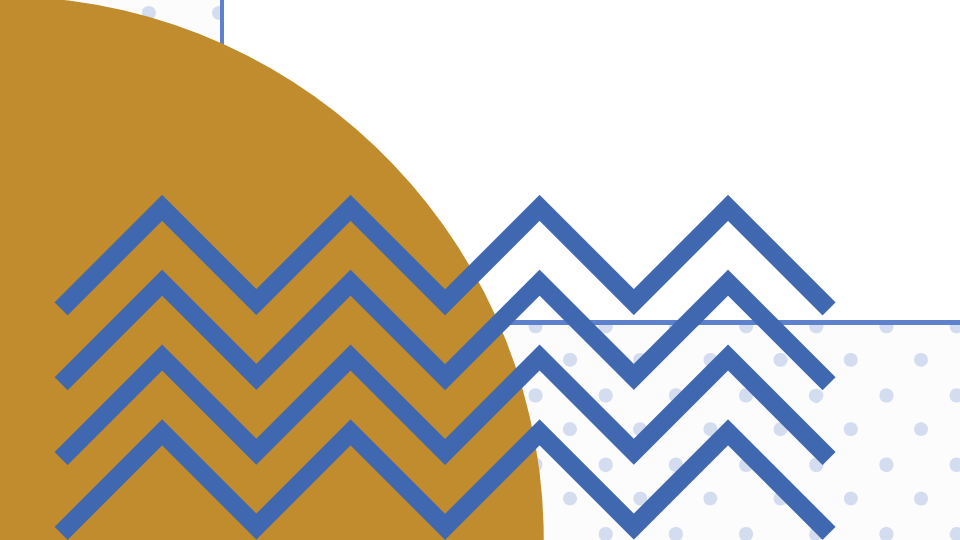


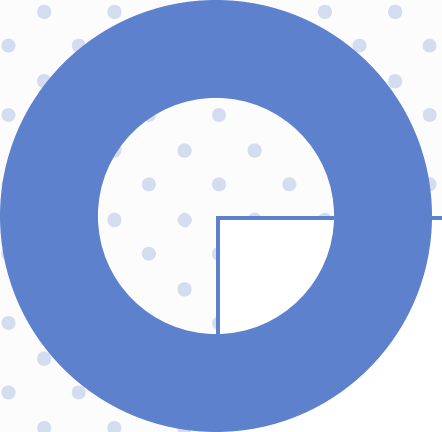
A DB-LINEAR PROGRAMMABLE GAIN AMPLIFIER (PGA) WITH MIXED-SIGNAL CONTROL





INTRODUCTION

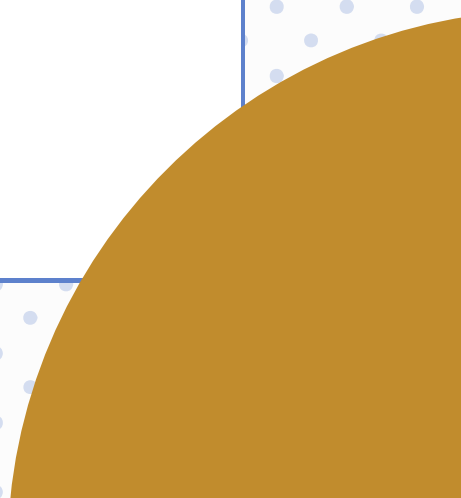
- 
- 
- The Need for VGAs: Variable Gain Amplifiers (VGAs) are critical in wireless receivers to maintain constant output power despite varying input signal levels.
 - Design Challenges: Maximizing dynamic range while minimizing power consumption is a primary trade-off.
 - Achieve a wide gain tuning range with precise dB-linear characteristics.
 - Target low-power IoT receiver application
 - Proposed Solution: A robust, cascaded unit cell-based PGA using MOS transistors in the sub-threshold region.
- 

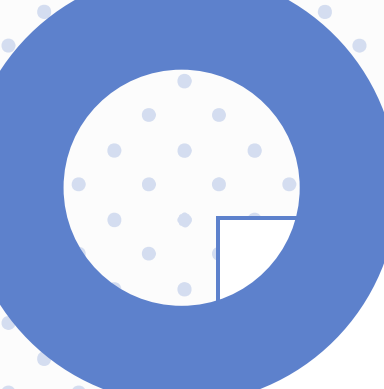


THE EVOLUTION OF GAIN CONTROL

- 
- **The Necessity of Variable Gain:** In wireless communications, input signals vary wildly in strength (Dynamic Range) depending on the distance from the transmitter.
 - **The Role of AGC:** Automatic Gain Control (AGC) loops are essential in receivers to maintain a constant output power.


Historical Shift:

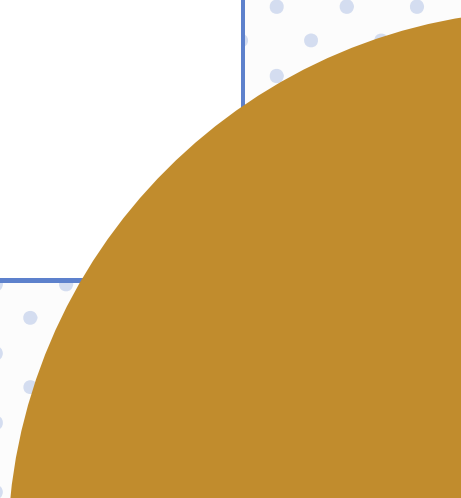- **Best of Both Worlds:** Unlike most chips that are either just digital or just analog, this one allows control via both digital computer codes and analog voltage, making it flexible for many different devices.
 - **Huge "Volume" Range:** It can handle a massive range of signal strengths (76 dB range)—amplifying very weak signals or handling strong ones without making errors
- 
- 

Gain tuning Circuit


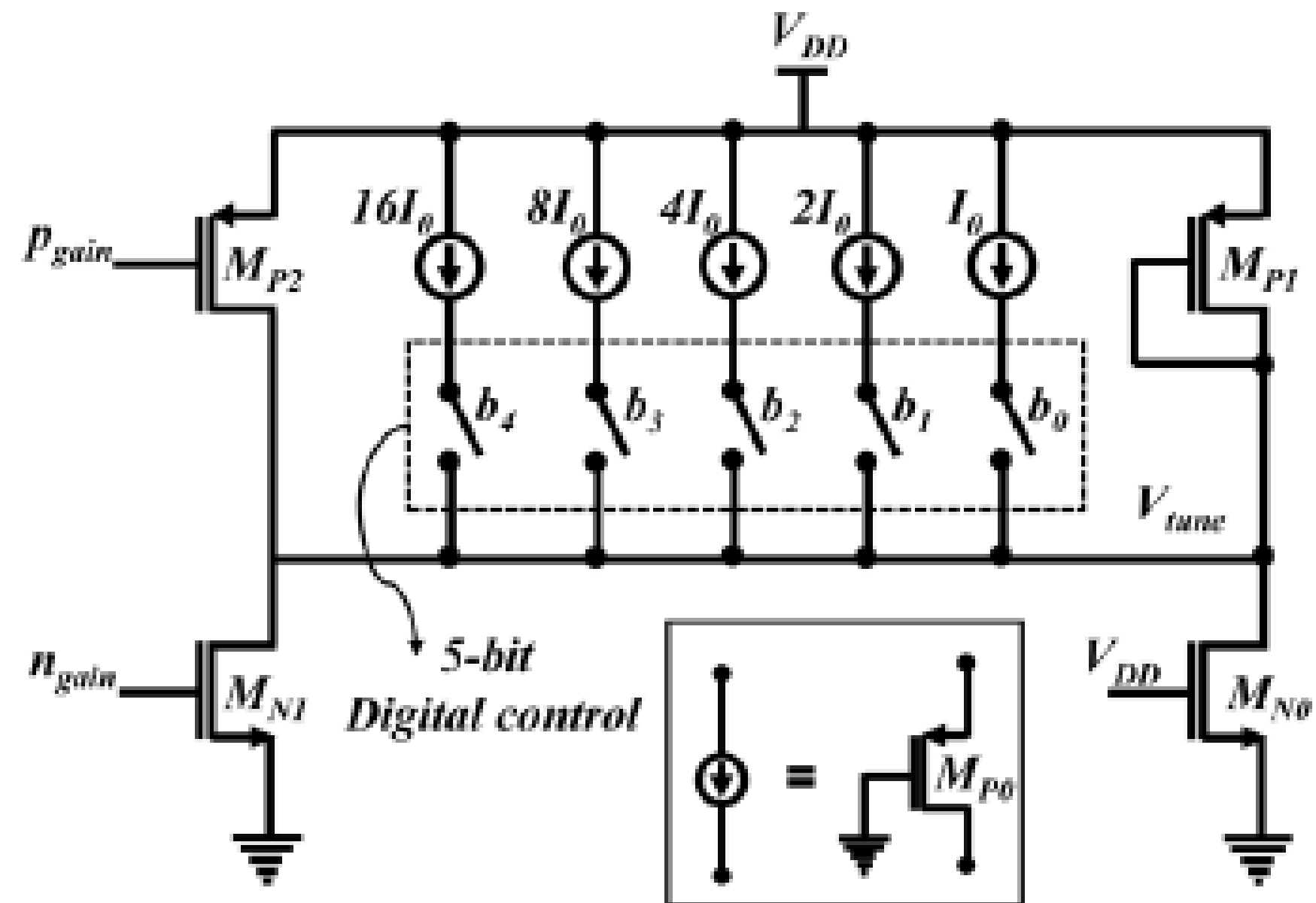


PGA unit cell and Bias circuit

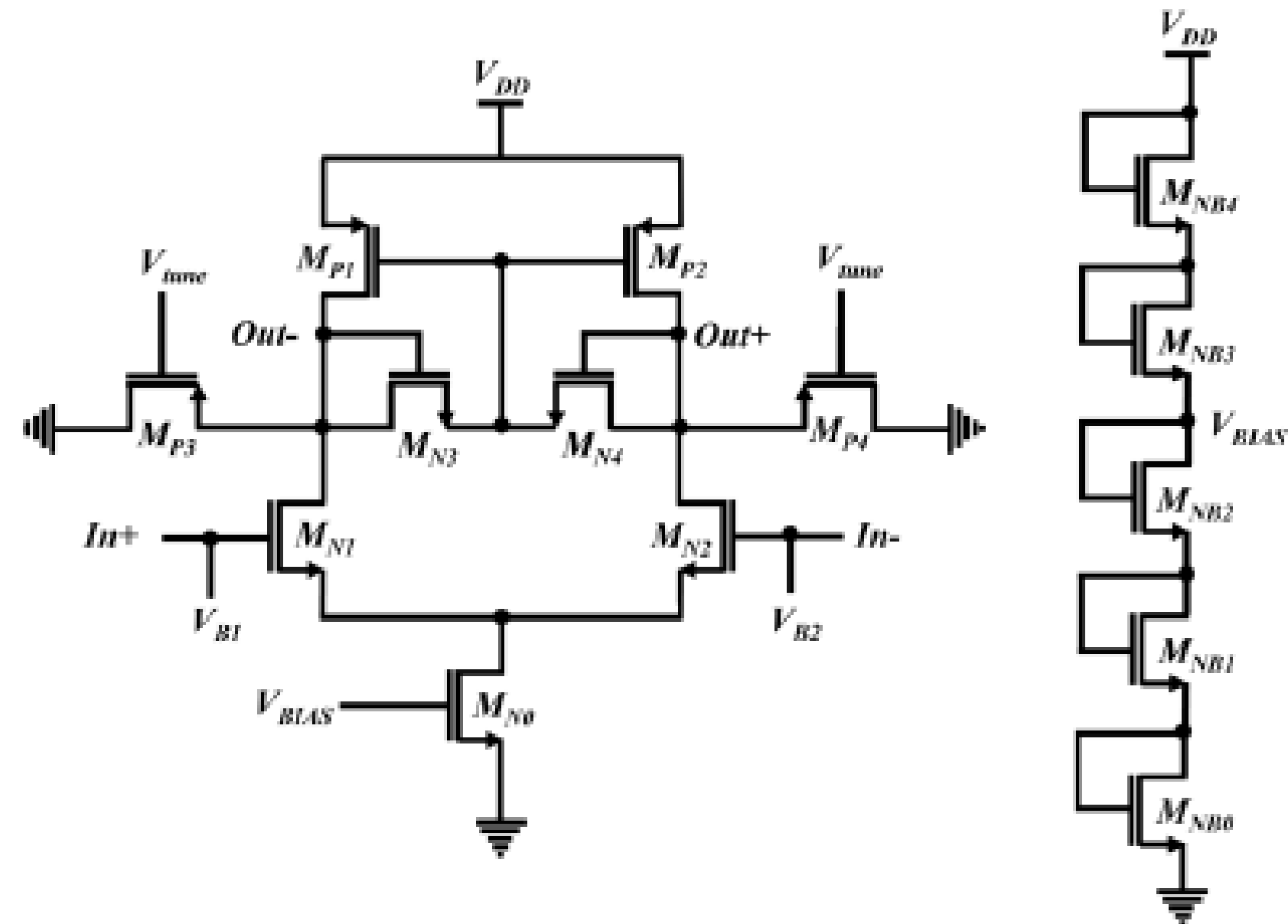

Pgain= 1.1V
ngain=0V
Vbw=800mv
Vin_dc=562mv
Vtune=150mv-450mv
V_bias=590mv

DCOC and Buffer circuit

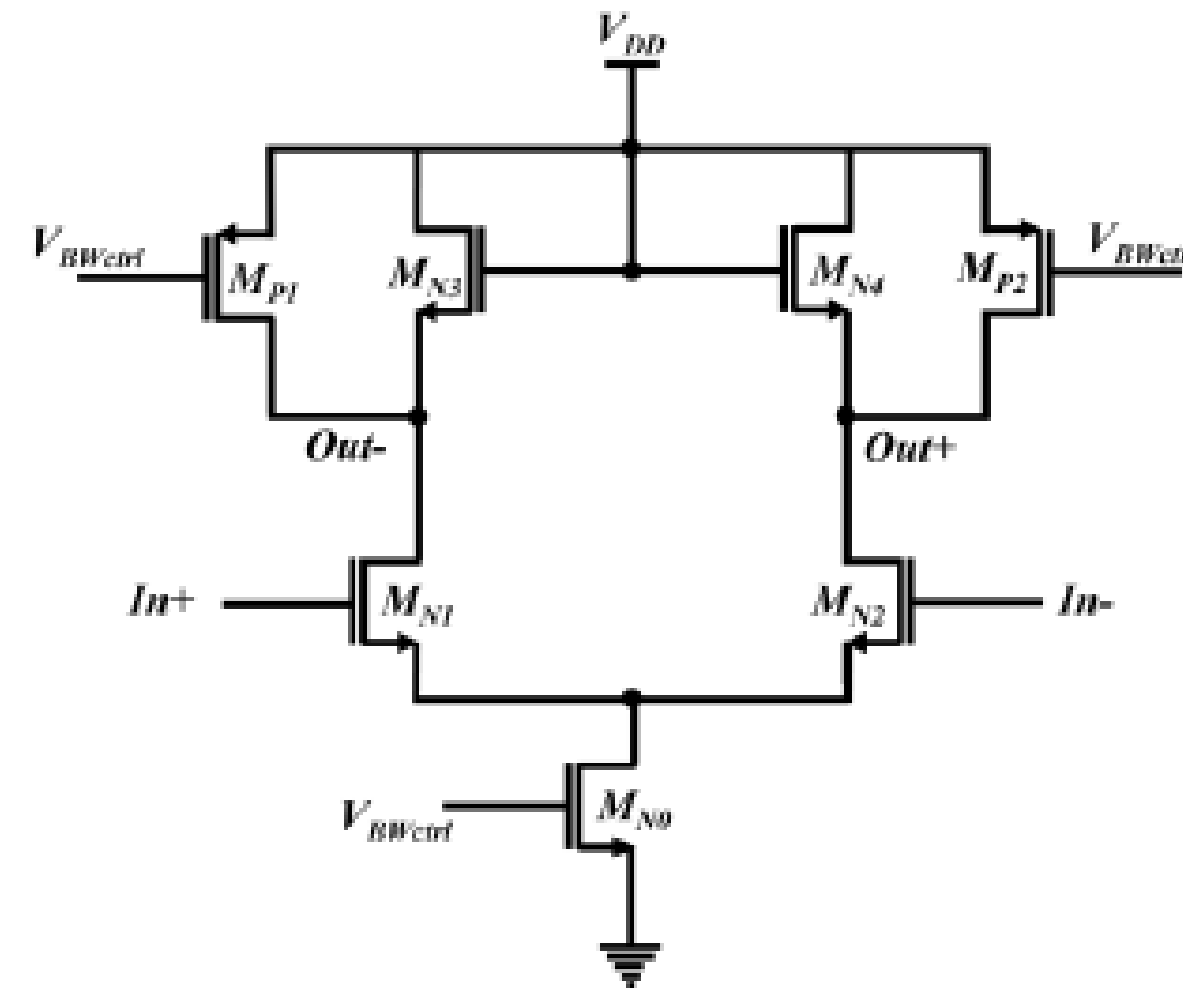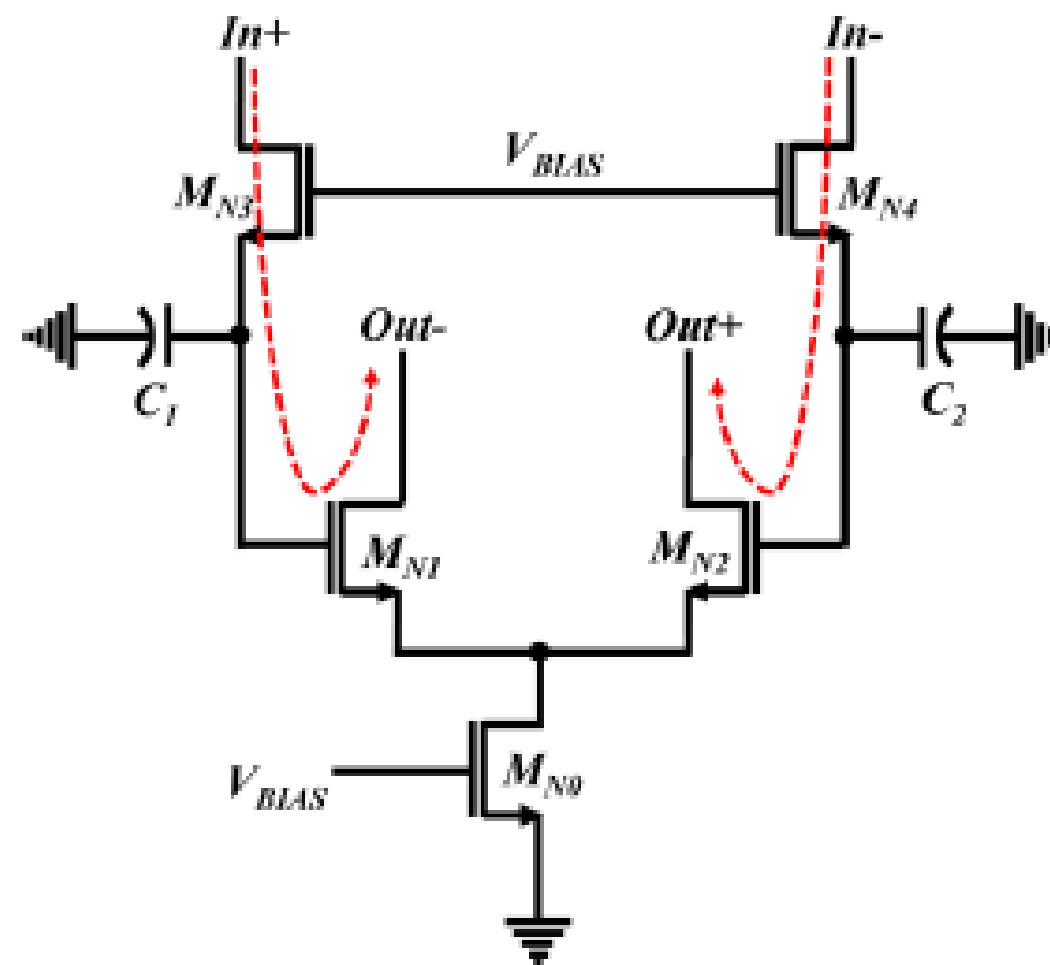

Pgain= 1.1V


ngain=0V

Vbw=800mv

Vin_dc=562mv


Vtune=150mv-450mv

V_bias=590mv

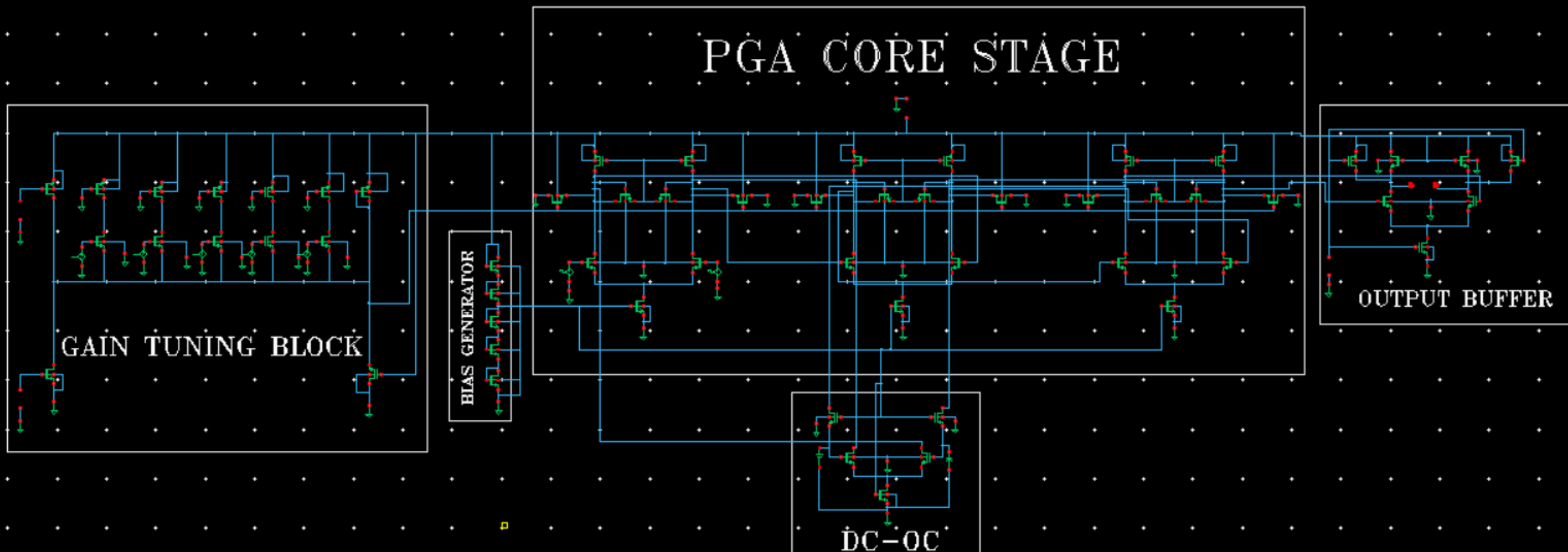


Observation and Results

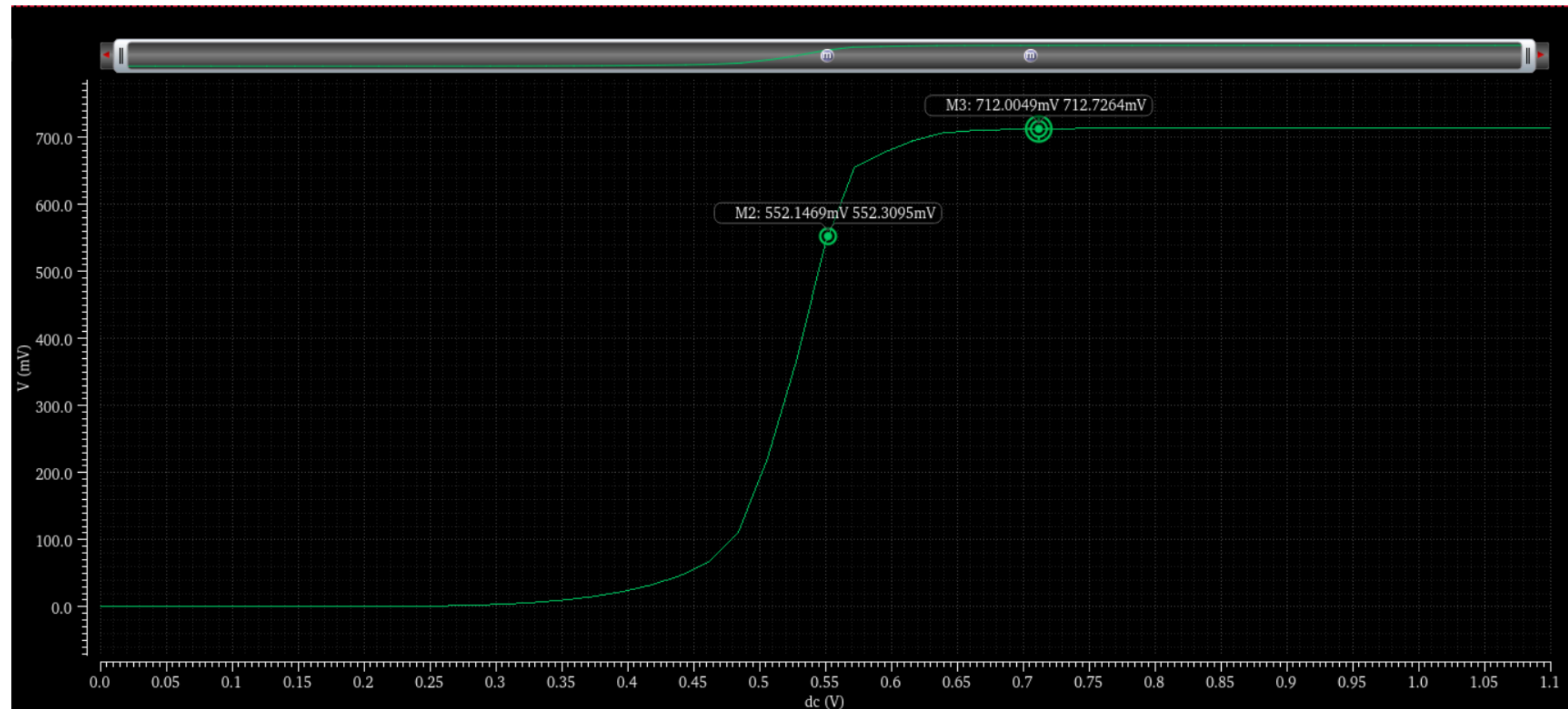Transfer Characteristics of Single cell PGA :




Observation and Results

Bode Plot of single PGA :

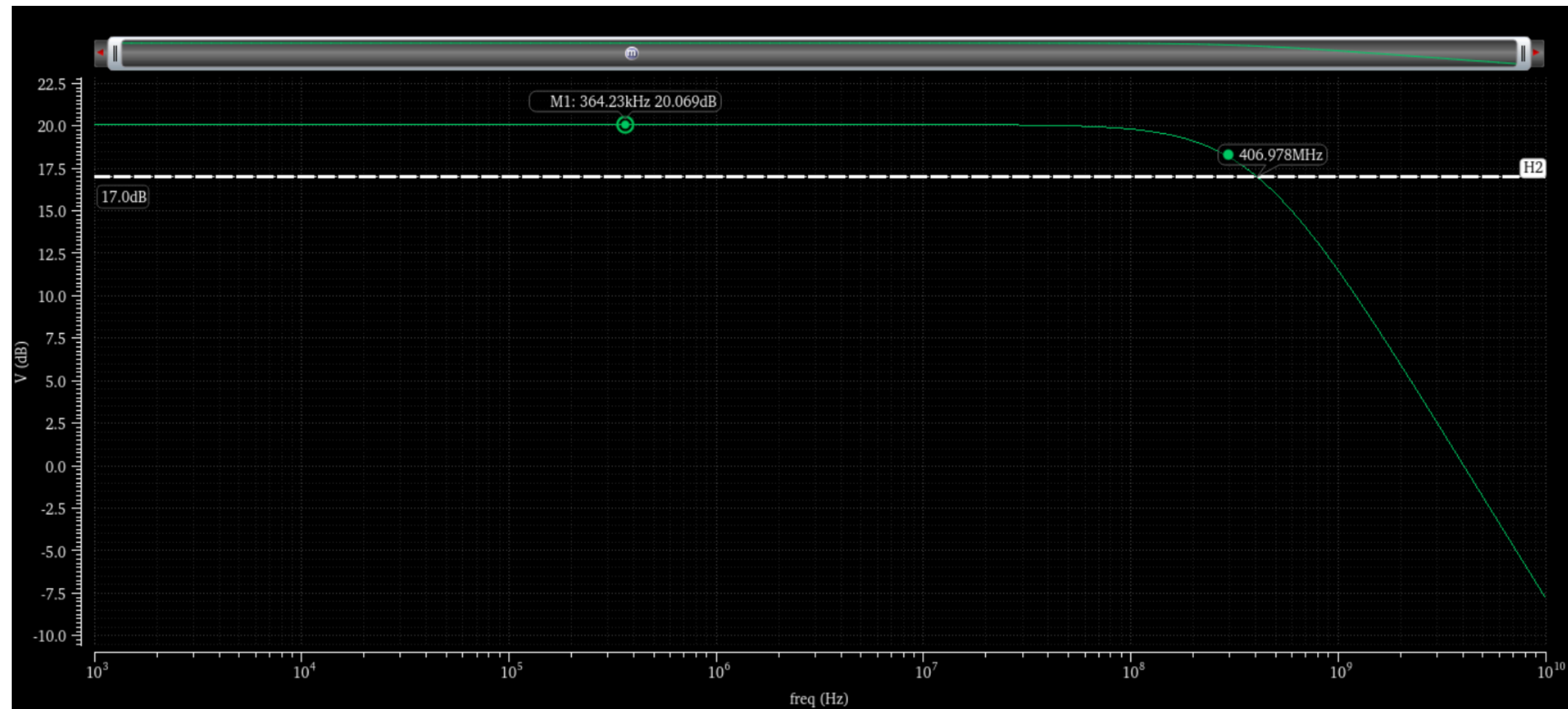


Observation and Results

3 Stage PGA Bode Plot :

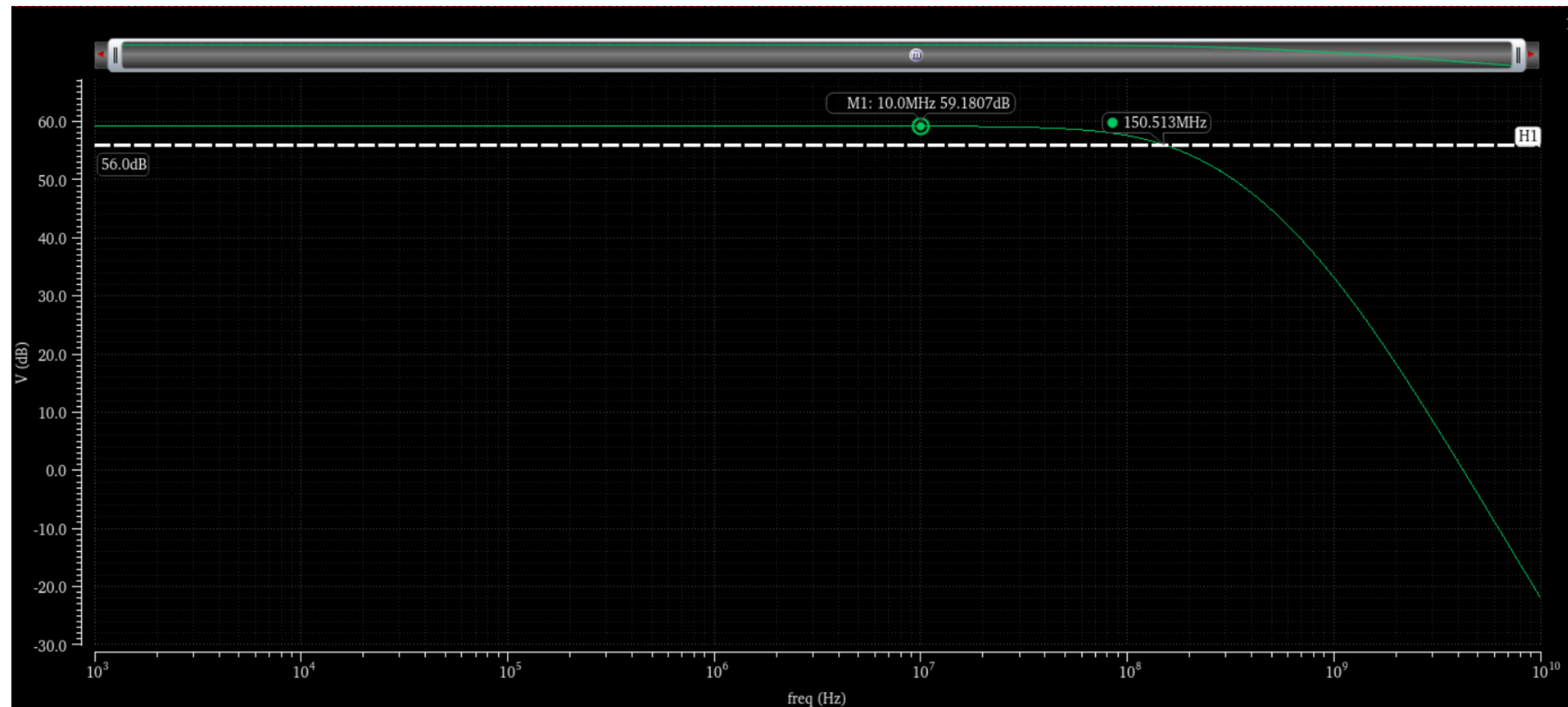


Observation and Results

Output waveforms of Binary (b'11111):

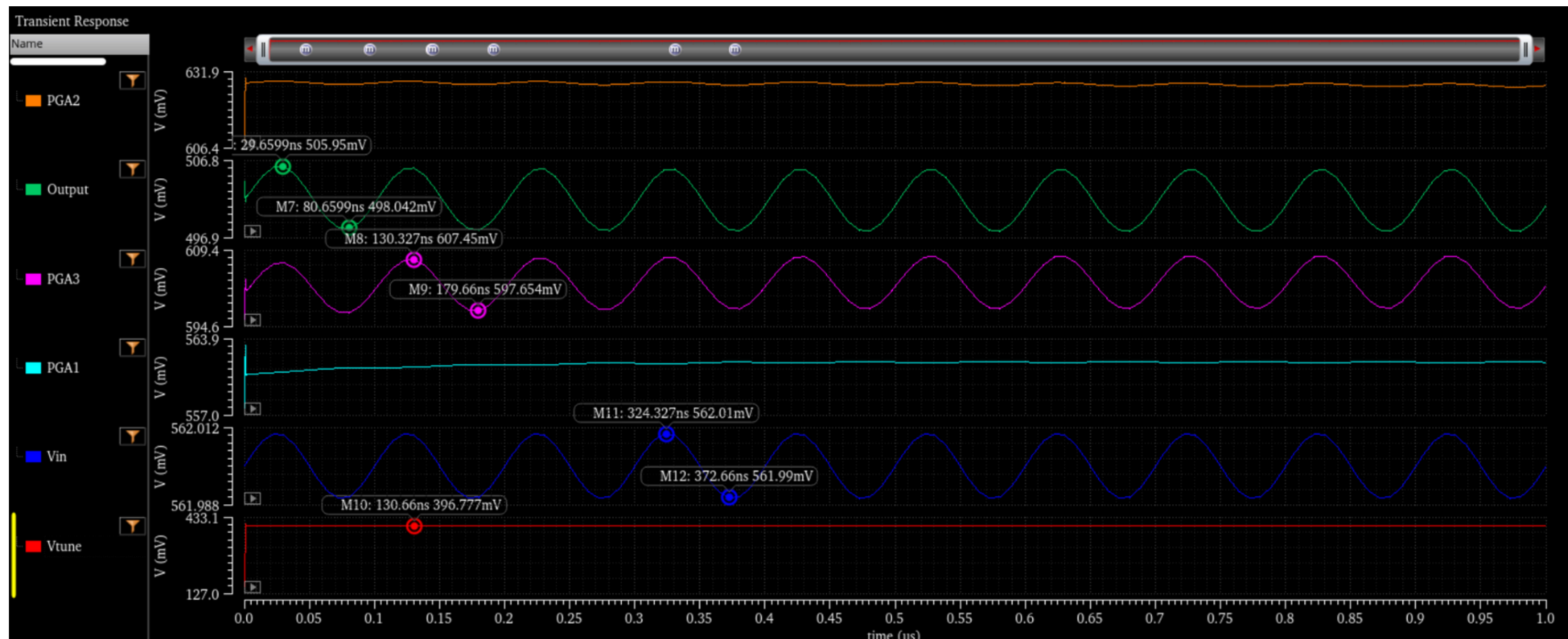


Observation and Results

Output waveforms of Binary (b'11111):

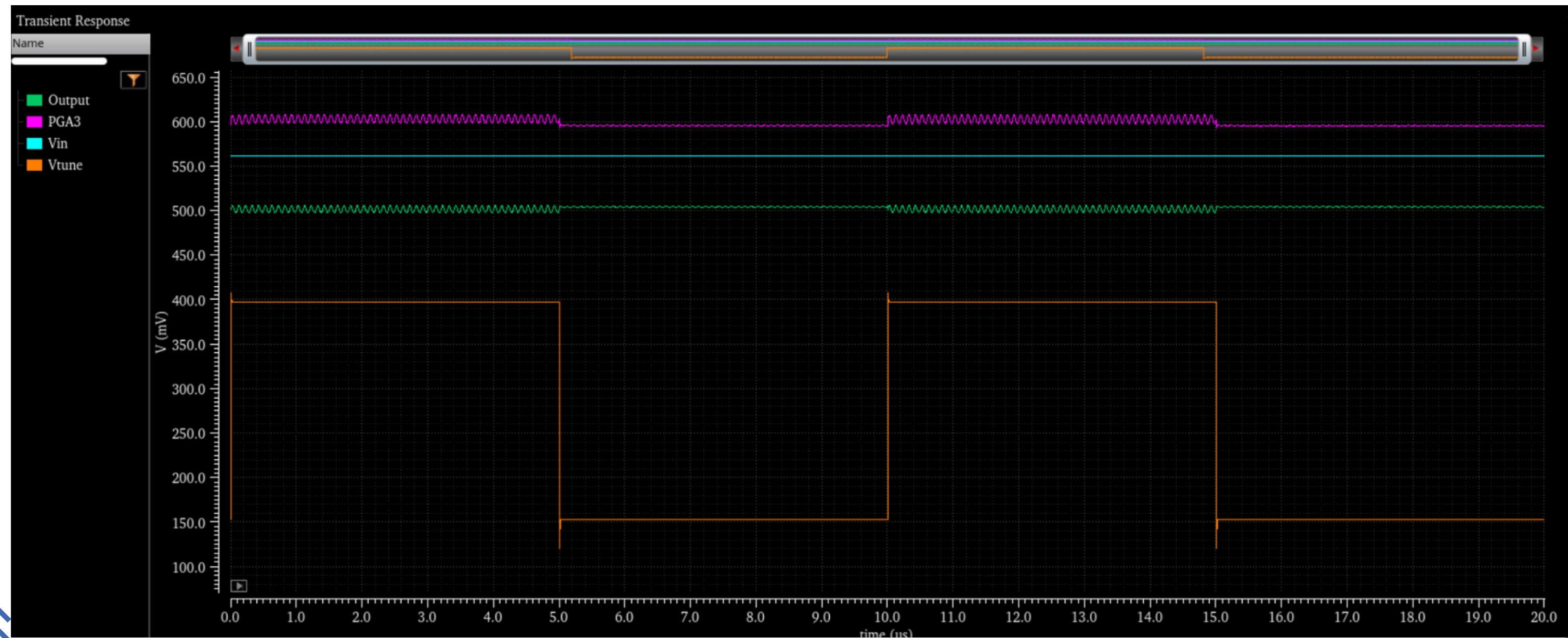


Observation and Results

Output waveforms of Binary (b'00100):

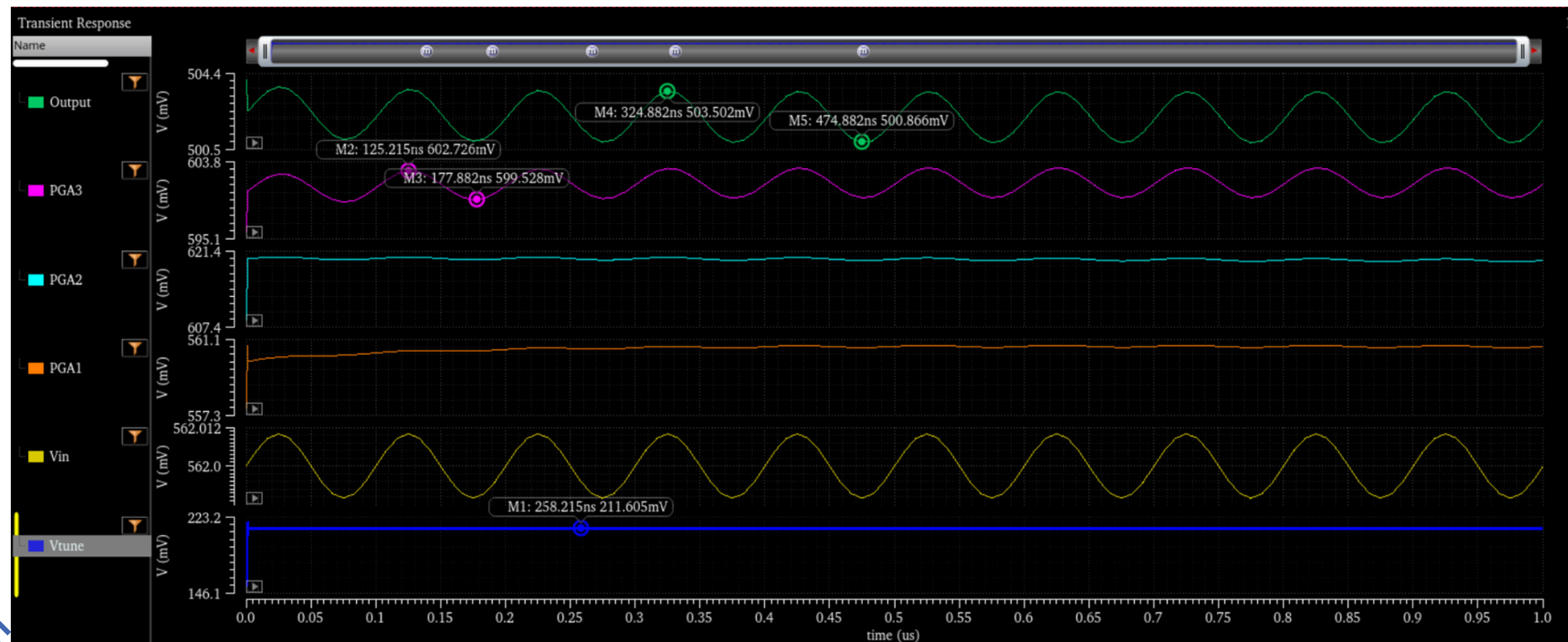


Observation and Results

Output waveforms of Binary (b'00100):

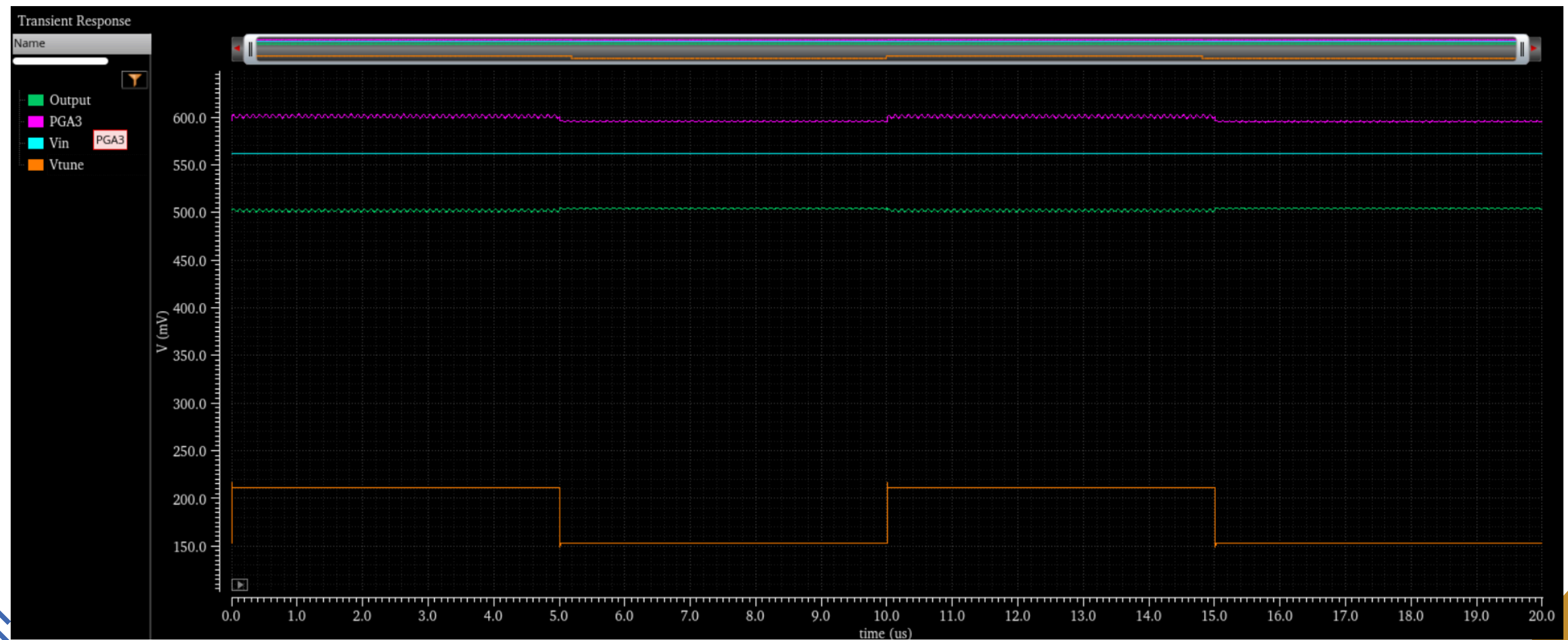


Observation and Results

Output waveforms of Binary (b'00000):

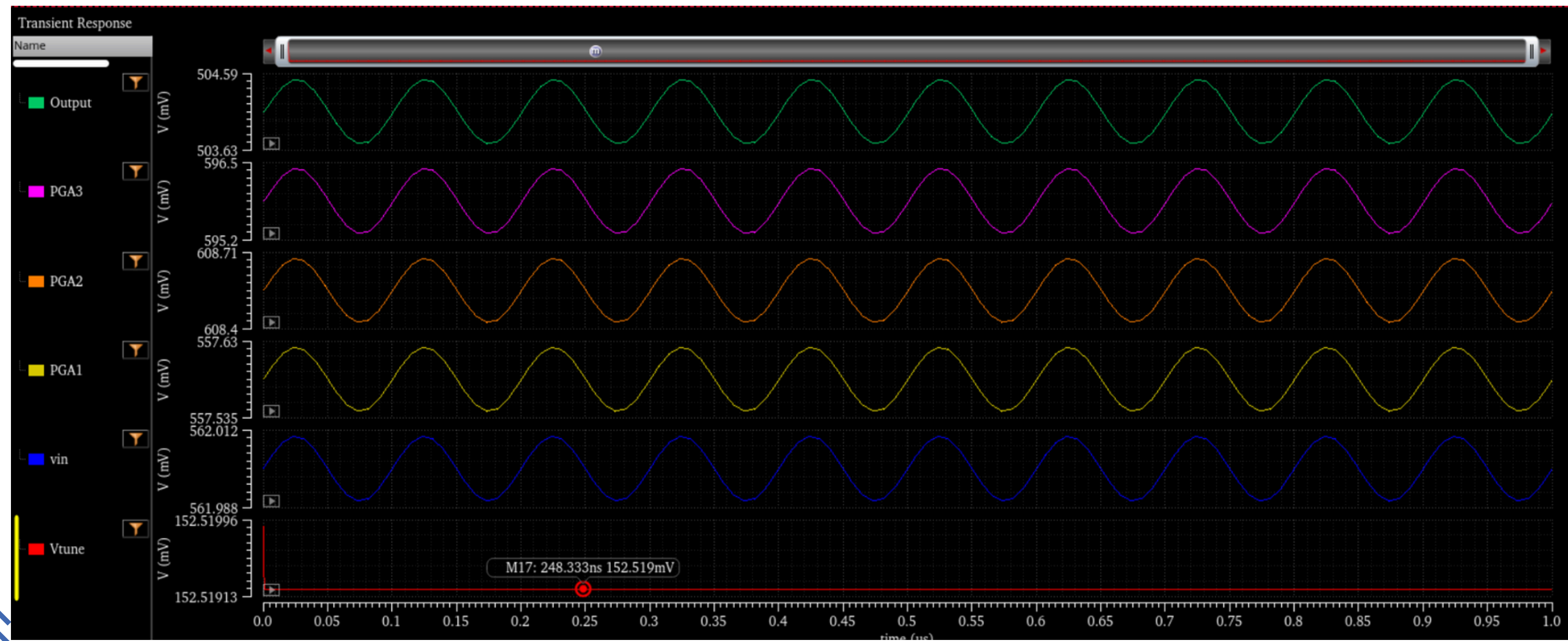

Observation and Results

Output waveforms of Binary (b'00000):

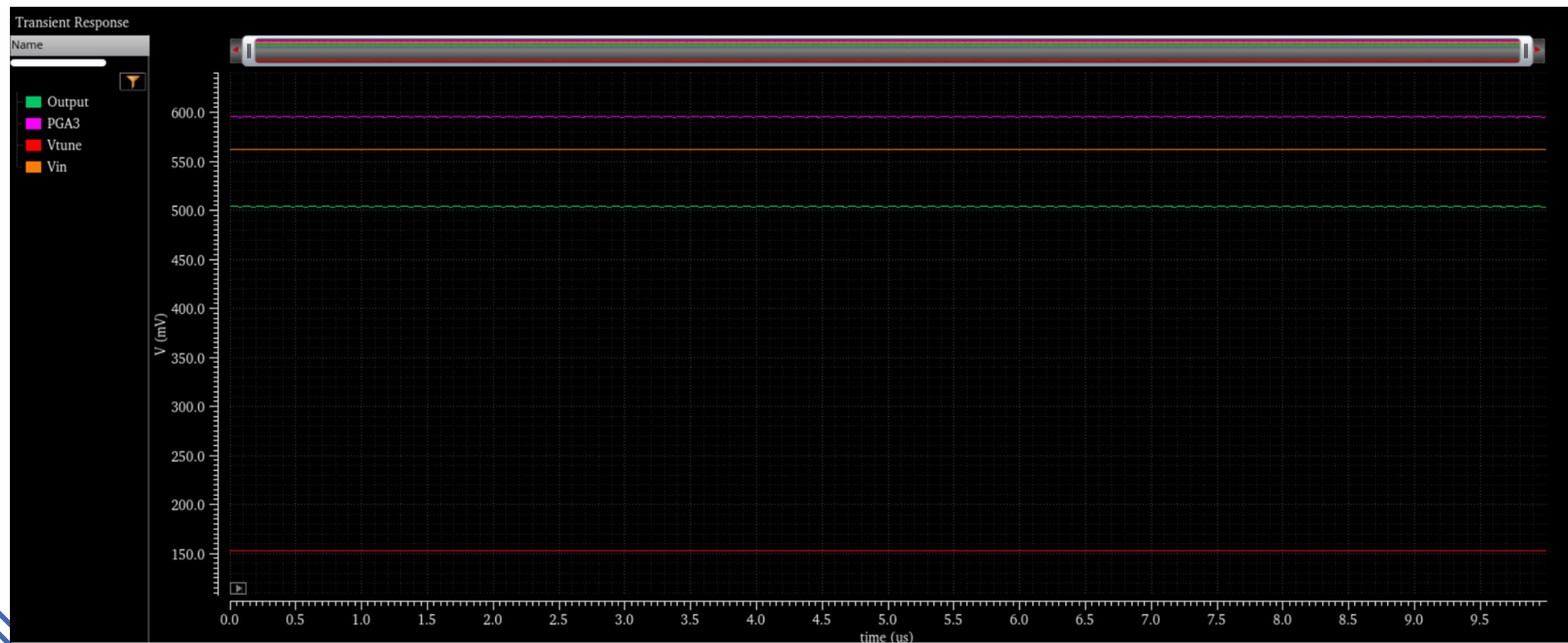

Observation and Results

Bode plot of 3 stage complete PGA circuit

